


ECSE-487
COMPUTER ARCHITECTURE
LABORATORY
Assignment #2

Andrei Purcarus Craciun
260631911

February 13, 2017




Ripple-carry Frequency Synthesizer

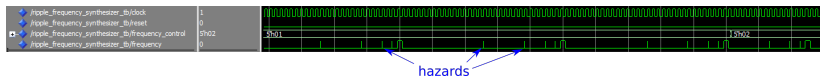- ▶ Data hazards on Cout
- ▶ Add a register to eliminate hazards at output



Ripple-carry Frequency Synthesizer


► Results

   

Ripple-carry Frequency Synthesizer




- ▶ Only divisors of clock rate can be generated exactly
- ▶ Other frequencies experience jitter
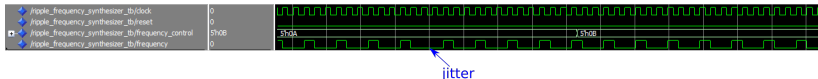
$$f_{out} = frequency_control * \frac{f_{clk}}{N}$$



Pipelined Frequency Synthesizer

► Results

   



Pipelined Frequency Synthesizer

- ▶ Synthesis results
- ▶ Pipelining has more impact with higher N

| | N = 5 | N = 32 |
|---------------------|--------------|---------------|
| ripple-carry | 142.71 MHz | 112.23 MHz |
| pipelined | 149.37 MHz | 144.01 MHz |

FSK Modulator

► Results

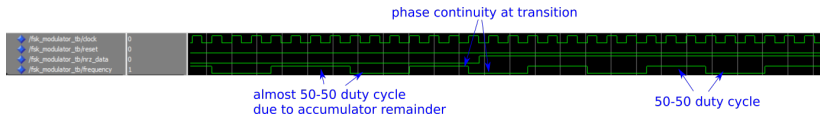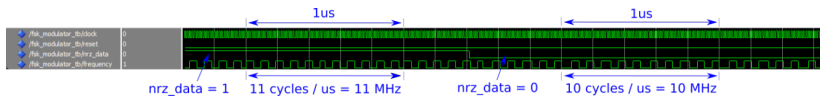

Analog Waveform Generator

- ▶ Sine wave shifted to $[0, 256)$
- ▶ Results

$$128(1 + \sin(\frac{2\pi}{10}t)), t = 0, 1, \dots, 9$$

