

# ECSE-487

## COMPUTER ARCHITECTURE

### LABORATORY


### Assignment #2

Andrei Purcarus Craciun  
260631911

February 13, 2017



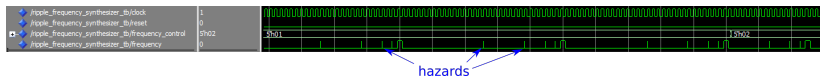
# Ripple-carry Frequency Synthesizer

- ▶ Data hazards on Cout
- ▶ Add a register to eliminate hazards at output



# Ripple-carry Frequency Synthesizer

## ► Results

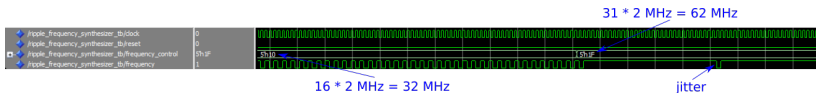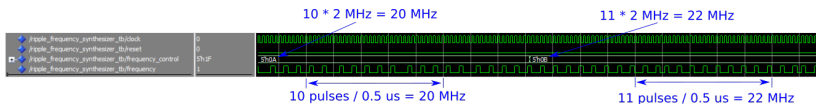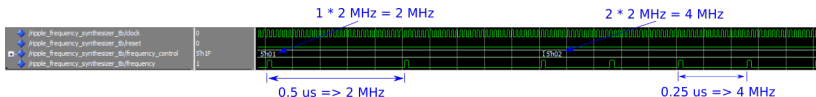

# Ripple-carry Frequency Synthesizer

- ▶ Only divisors of clock rate can be generated exactly
- ▶ Other frequencies experience jitter

Table: Input of 0x0A




0	8	6	4	2	0
10	18	16	14	12	10
20	28	26	24	22	20
30	38	36	34	32	30
40					40



jitter

# Pipelined Frequency Synthesizer

## ► Results

  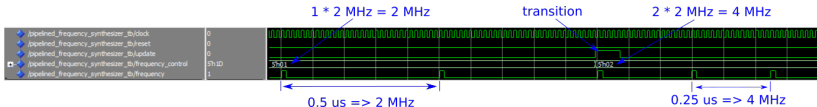



# Pipelined Frequency Synthesizer

- ▶ Synthesis results
- ▶ Pipelining has more impact with higher N

	<b>N = 5</b>	<b>N = 32</b>
<b>ripple-carry</b>	142.71 MHz	112.23 MHz
<b>pipelined</b>	149.37 MHz	144.01 MHz

# FSK Modulator

## ► Results

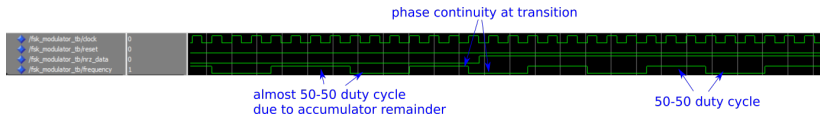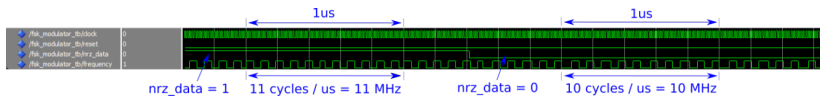

# Analog Waveform Generator

- ▶ Sine wave shifted to  $[0, 256)$
- ▶ Results

$$128(1 + \sin(\frac{2\pi}{10}t)), t = 0, 1, \dots, 9$$

